
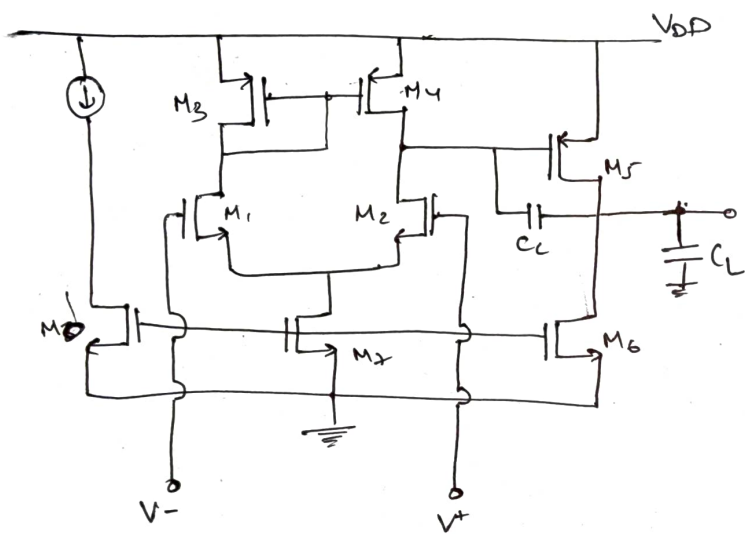


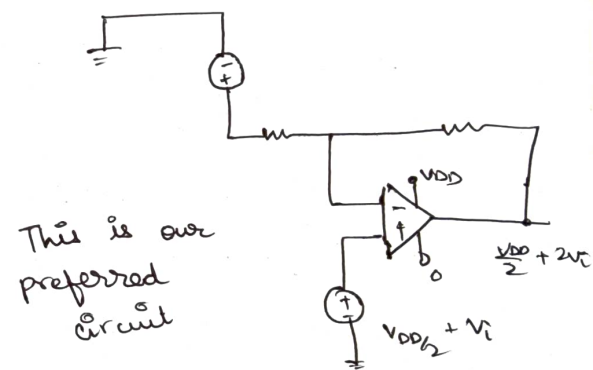

Circuit Diagram

Assumptions & Given Informations



This is our preferred circuit

Specifications

- i) at least 40 dB (let's take 60 dB) of DC gain
- ii) GBW = 5 MHz
- iii) PM $\geq 60^\circ$
- iv) Slew Rate $\geq 10 \text{ V}/\mu\text{sec}$
- v) ICNR (+) = 1.6 V
ICNR (-) = 0.8 V
- vi) let's take $C_L = 10 \text{ pF}$
- vii) $V_{DD} = 1.8 \text{ V}$
- viii) $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ (initially)
 $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$ (initially)

Calculations :-

Slew Rate $\frac{I_s}{C_c}$

and for $\geq 60^\circ$ Phase Margin

$$C_c = 0.4 C_L = 4 \text{ pF}$$

$$I_s = 10 \times 10^6 \times 4 \times 10^{-12}$$

$$I_s = 40 \mu\text{A}$$

M_1 & M_2

$$g_{m1} = \text{GBW} \cdot C_c \cdot 2\pi$$

$$g_{m1} = 5 \times 10^6 \times 2\pi \times 4 \times 10^{-12}$$

$$g_{m1} = 40\pi \mu\text{S}$$

$$g_{m1} = 125 \mu\text{S}$$

$$g_{m1} = \sqrt{I_{D1} \mu_n C_{ox} \left(\frac{W}{L} \right)}$$

$$\frac{W}{L} = \frac{(g_{m1})^2}{\mu_n C_{ox} I_{D2}} = \frac{(125)^2}{230 \times 40} = 1.69$$

$$\boxed{\frac{W}{L} = 1.69}$$

From the Rough slide we get

$$\sqrt{\frac{I_{D5}}{\beta_3}} = V_{DD} - |V_{th3}| + V_{th1} - V_{in} \text{ max}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{I_S}{\mu_p C_{ox} (V_{DD} - |V_{th3}| + V_{th1} - V_{in \text{ max}})^2}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{40 \mu A}{100 \frac{\mu A}{V} (1.8 - 0.37 + 0.31 - 1.6)^2}$$

$$\boxed{\left(\frac{W}{L}\right)_{3,4} = 20.40}$$

Negative CMRR use for the second one.

$$V_{dsat7} = 0.8 - 0 - \sqrt{\frac{I_{D7}}{\beta_1}} = V_{th}$$

Overdrive voltage.

$$V_{dsat7} = 0.8 - \sqrt{\frac{40}{230 \times 1.69}} = 0.37$$

$$V_{dsw7} = 0.8 - 0.37 = 0.1$$

$$\boxed{V_{dsat7} = 0.12V}$$

$$\left(\frac{W}{L}\right)_7 = \frac{230 \mu A}{\mu_n C_{ox} V_{dsat7}^2}$$

$$\left(\frac{W}{L}\right)_7 = \frac{2 \times 40 \mu A}{280 \frac{\mu A}{V} \times 0.12 V}$$

$$\left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_6 = 2.9$$

M_0 and M_5 from current mirror but given we have to have $1/10^{th}$ of the I_7 in the $\left(\frac{W}{L}\right)_{M_0}$

$$\left(\frac{W}{L}\right)_{M_0} = \frac{1}{10} (2.9) = \underline{0.29}$$

$$\frac{12 \mu}{L} = 0.29$$

$$L = \frac{12 \mu}{0.29} \text{ Rough}$$

for Reasonable Phase Margin ($\sim 60^\circ$)

$$g_{m5} = 2.2 g_{m4} \left(\frac{C_L}{C_c}\right)$$

$$\text{and } g_{m5} \gg 10 g_{m1}$$

$$V_{SG4} = V_{SE} = 5$$

$$\left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_4 \left(\frac{g_{m5}}{g_{m4}}\right)$$

calculations of I_{D6}

$$g_{m6} = \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_6 I_{D6}}$$

$$g_{m6}^2 = 2 \mu_p C_{ox} \left(\frac{W}{L}\right)_6 I_{D6}$$

$$I_{D6} = \frac{(g_{m6})^2}{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_6}$$

$$P_2 = \frac{g_{m5}}{2\pi C_L} \text{ Comes purely from the second stage}$$

$$GBW = 5 \text{ MHz}$$

$$P_2 \geq 2.2 \times 5 \text{ MHz} = 11 \text{ MHz}$$

$$P_2 \approx \frac{g_{m5}}{2\pi C_L}$$

$$11 \times 10^6 = \frac{g_{m5}}{2\pi \times (10 \times 10^{-6})}$$

$$g_{m5} \geq 691 \text{ mS}$$

Now since overdrive in both are same:-
 $(V_{s6} - V_{TH})$ is same for both M_4 & M_5

$$g_{m4} = \sqrt{2\mu_n C_{ox} (W/L)_4 I_{D4}}$$

$$g_{m4} = \sqrt{2 \times 100 \mu \times 20.45 (20) \mu \text{A}}$$

$$g_{m4} = 286 \text{ mS}$$

$$\Delta V_{OH} = \frac{2I_{D4}}{g_{m4}} = \frac{2(20) \mu \text{A}}{286 \text{ mS}}$$

$$\Delta V_{OH} = 0.14 \text{ V}$$

So for better phase margin we already got $g_{m5} \geq 691 \text{ mS}$

we must have $\Delta V_S = \Delta V_D = 0.14V$

$$g_{mS} = \frac{2I_{DS}}{V_{ovS}}$$

$$I_{DS} = \frac{891/\mu A \times 0.14}{2}$$

$$I_{DS} = 48.37 \mu A$$

lets Assume ($\approx 55 \mu A$)

$$\left(\frac{W}{L}\right)_S = 20.45 \times 2.75 = 56.2375$$


$$\begin{aligned} W &= 25.551 \mu m \\ L &= 0.45 \mu m \end{aligned}$$


Now

M6 must be able to pull the much current

$\left(\frac{55}{4}\right)$ multiplier

$$\frac{55}{4} \times 1.69 \approx \frac{55}{4} \times 2 = \underline{\underline{27.5}}$$

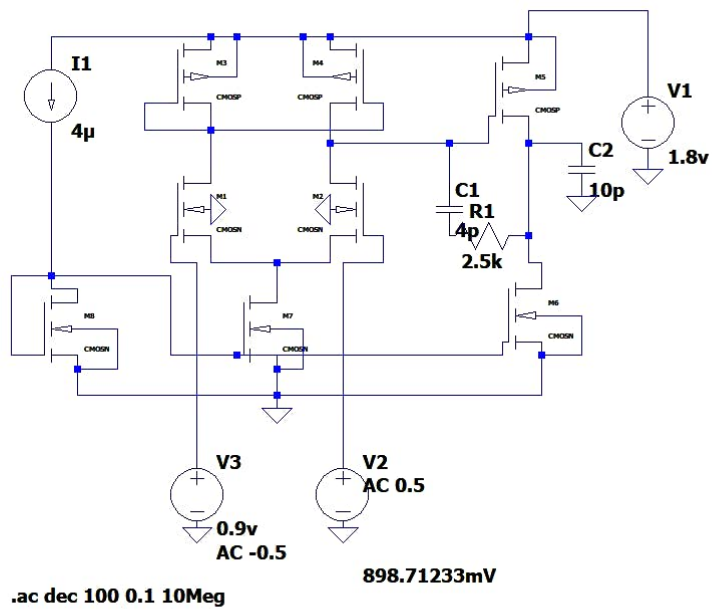

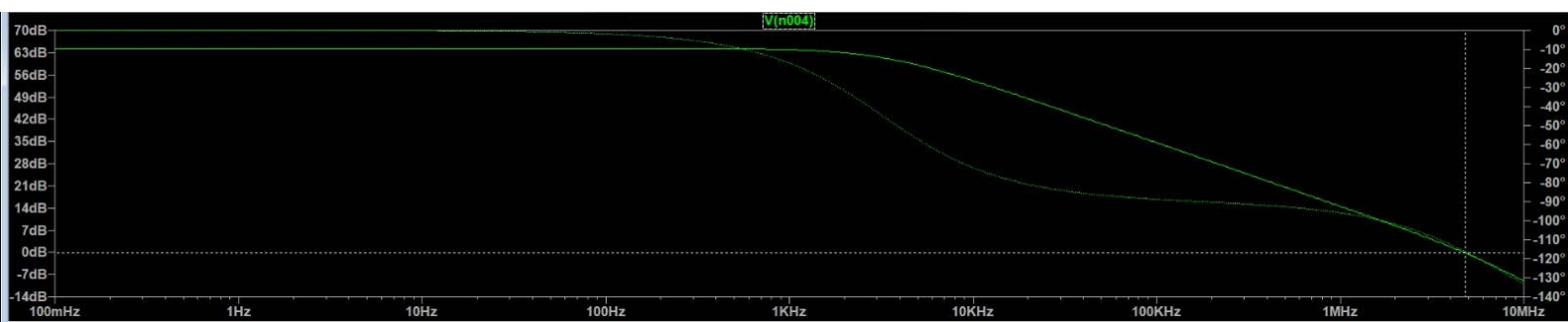

Cursor 1

V(n004)

Freq:	4.7962176MHz	Mag:	-252.70729mdB	☒
		Phase:	-116.34628°	☐
		Group Delay:	12.406939ns	☐

Cursor 2

Freq:	-- N/A--	Mag:	-- N/A--	☐
		Phase:	-- N/A--	☐
		Group Delay:	-- N/A--	☐

Ratio (Cursor2 / Cursor1)

Freq:	-- N/A--	Mag:	-- N/A--
		Phase:	-- N/A--
		Group Delay:	-- N/A--

V(n001) :	1.8	voltage
V(n002) :	1.15744	voltage
V(n003) :	1.19874	voltage
V(n004) :	0.902604	voltage
V(n005) :	0.9	voltage
V(n006) :	0.902604	voltage
V(n007) :	0.901302	voltage
V(n008) :	0.0849597	voltage
V(n009) :	0.557781	voltage
V(n010) :	0.9	voltage
I(C1) :	1.18453e-24	device_current
I(C2) :	9.02604e-24	device_current
I(I1) :	4e-06	device_current
I(R1) :	0	device_current
I(R2) :	1.30188e-10	device_current
I(R3) :	1.30188e-10	device_current
I(V1) :	-0.000106646	device_current
I(V2) :	0	device_current
I(V4) :	1.30188e-10	device_current
Ib(M1) :	-1.26203e-12	device_current
Ib(M2) :	-1.30332e-12	device_current
Ib(M3) :	6.52559e-13	device_current
Ib(M4) :	6.11263e-13	device_current
Ib(M5) :	9.07396e-13	device_current
Ib(M6) :	-9.12604e-13	device_current
Ib(M7) :	-9.45853e-14	device_current
Ib(M8) :	-5.67781e-13	device_current

Ib (M8) :	-5.67781e-13	device_current
Id (M1) :	2.79511e-05	device_current
Id (M2) :	2.78263e-05	device_current
Id (M3) :	2.79511e-05	device_current
Id (M4) :	2.78263e-05	device_current
Id (M5) :	4.68687e-05	device_current
Id (M6) :	4.68686e-05	device_current
Id (M7) :	5.57773e-05	device_current
Id (M8) :	4e-06	device_current
Ig (M1) :	0	device_current
Ig (M2) :	0	device_current
Ig (M3) :	-0	device_current
Ig (M4) :	-0	device_current
Ig (M5) :	-0	device_current
Ig (M6) :	0	device_current
Ig (M7) :	0	device_current
Ig (M8) :	0	device_current
Is (M1) :	-2.79511e-05	device_current
Is (M2) :	-2.78263e-05	device_current
Is (M3) :	-2.79511e-05	device_current
Is (M4) :	-2.78263e-05	device_current
Is (M5) :	-4.68687e-05	device_current
Is (M6) :	-4.68686e-05	device_current
Is (M7) :	-5.57773e-05	device_current
Is (M8) :	-4e-06	device_current

